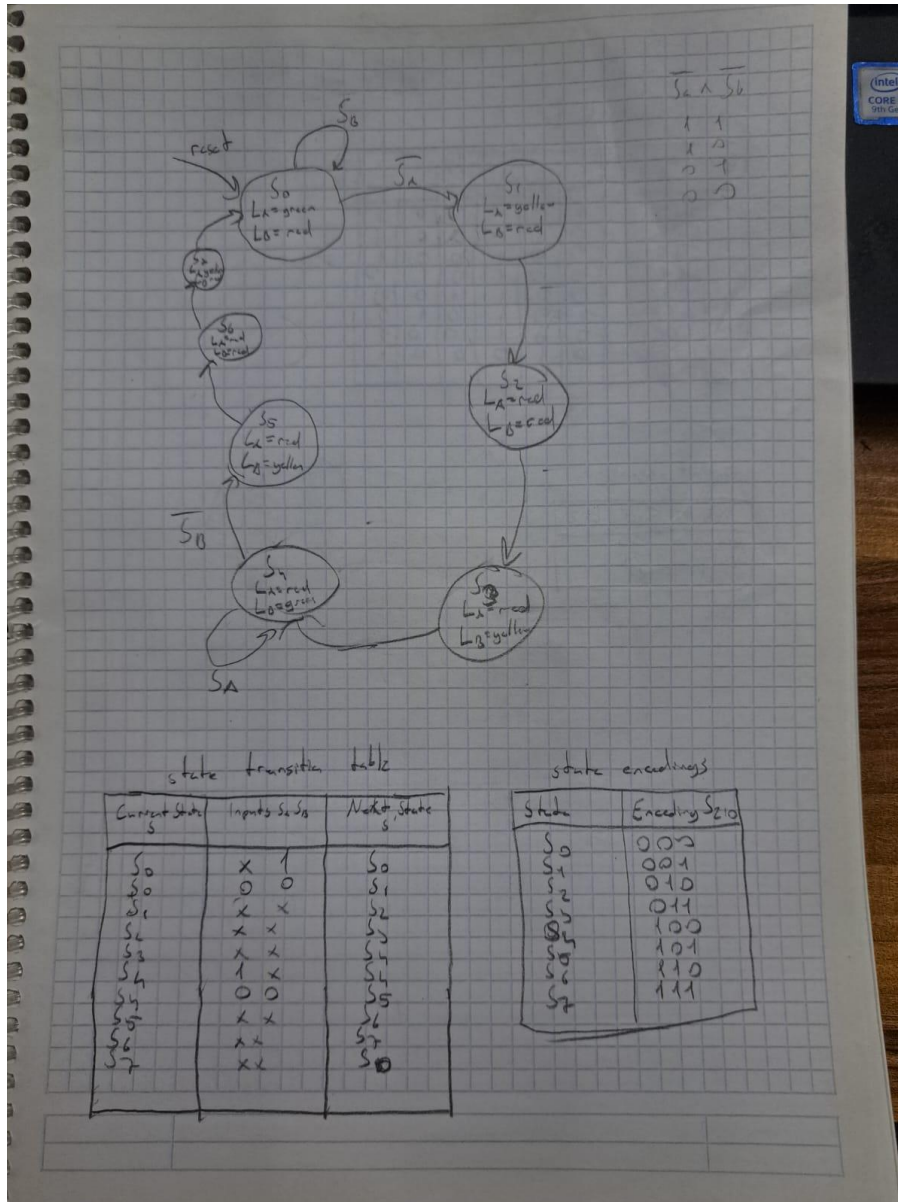


CS223 LAB5

Altay İlker Yiğitel

22203024

CS223 sec: 01




Output table

Current state S2S1	Outputs					
	L _{A00}	L _{A01}	L _{A10}	L _{A01}	L _{B00}	L _{B01}
000	1	0	0	0	0	1
001	0	1	0	0	0	1
010	0	0	1	0	0	1
011	0	0	1	0	1	0
100	0	0	1	1	0	0
101	0	0	1	0	1	0
110	0	0	1	0	0	1
111	0	1	0	0	0	1

Output equations

Output	Encoding L1:0
green	00
yellow	01
red	11

 2 flip flops are needed as there are 2 important states L_A=green L_B=red and L_A=red and L_B=green



System verilog code

Traffic Light System

module traffic(

```
    input SA,  
    input SB,  
    output LA_green,  
    output LA_yellow,  
    output LA_red,  
    output LB_green,  
    output LB_yellow,  
    output LB_red,  
    input clk  
);
```

```
typedef enum logic [3:0] {  
    BOTH_RED1,  
    BOTH_RED2,  
    LA_GREEN,  
    LB_GREEN,  
    LA_YELLOW1,  
    LB_YELLOW1,  
    LA_YELLOW2,  
    LB_YELLOW2  
} state_t;
```

```
state_t current_state, next_state;  
logic [1:0] counter;
```

```
initial begin  
    current_state = LA_GREEN;  
    counter = 0;
```

```
    LA_green = 1; LA_yellow = 0; LA_red = 0;
    LB_green = 0; LB_yellow = 0; LB_red = 1;
end
```

```
always @(posedge clk) begin
    case (current_state)
        LA_GREEN: begin
            if (!(SA && SB)) begin
                next_state = LA_GREEN;
            end else begin
                next_state = LA_YELLOW1;
            end
        end
        LB_GREEN: begin
            if (!(SA && SB)) begin
                next_state = LB_GREEN;
            end else begin
                next_state = LB_YELLOW1;
            end
        end
        BOTH_RED1: begin
            if (counter == 3) begin
                next_state = LA_YELLOW2;
            end else begin
                next_state = BOTH_RED1;
            end
        end
        BOTH_RED2: begin
            if (counter == 3) begin
```

```
        next_state = LB_YELLOW2;
    end else begin
        next_state = BOTH_RED2;
    end
end
LA_YELLOW1: begin
    if (counter == 3) begin
        next_state = BOTH_RED1;
    end else begin
        next_state = LA_YELLOW1;
    end
end
LB_YELLOW1: begin
    if (counter == 3) begin
        next_state = BOTH_RED2;
    end else begin
        next_state = LB_YELLOW1;
    end
end
LA_YELLOW2: begin
    if (counter == 3) begin
        next_state = LB_GREEN;
    end else begin
        next_state = LA_YELLOW2;
    end
end
LB_YELLOW2: begin
    if (counter == 3) begin
        next_state = LA_GREEN;
```

```

        end else begin
            next_state = LB_YELLOW2;
        end
    end
endcase
end

always @(posedge clk) begin
    if (counter == 3) begin
        counter <= 0;
    end else begin
        counter <= counter + 1;
    end
end

case (next_state)
    BOTH_RED: begin
        LA_green = 0; LA_yellow = 0; LA_red = 1;
        LB_green = 0; LB_yellow = 0; LB_red = 1;
    end
    BOTH_YELLOW: begin
        LA_green = 0; LA_yellow = 1; LA_red = 0;
        LB_green = 0; LB_yellow = 1; LB_red = 0;
    end
    LA_GREEN: begin
        LA_green = 1; LA_yellow = 0; LA_red = 0;
        LB_green = 0; LB_yellow = 0; LB_red = 1;
    end
    LB_GREEN: begin
        LA_green = 0; LA_yellow = 0; LA_red = 1;

```

```

        LB_green = 1; LB_yellow = 0; LB_red = 0;
    end
    LA_YELLOW: begin
        LA_green = 0; LA_yellow = 1; LA_red = 0;
        LB_green = 0; LB_yellow = 0; LB_red = 1;
    end
    LB_YELLOW: begin
        LA_green = 0; LA_yellow = 0; LA_red = 1;
        LB_green = 0; LB_yellow = 1; LB_red = 0;
    end
endcase

current_state <= next_state;
end

endmodule

```

Testbench

```

module traffic_tb;

    input SA;
    input SB;
    input clk;

    output LA_green;
    output LA_yellow;
    output LA_red;

```

```
output LB_green;
```

```
output LB_yellow;
```

```
output LB_red;
```

```
traffic dut (
```

```
    .SA(SA),
```

```
    .SB(SB),
```

```
    .LA_green(LA_green),
```

```
    .LA_yellow(LA_yellow),
```

```
    .LA_red(LA_red),
```

```
    .LB_green(LB_green),
```

```
    .LB_yellow(LB_yellow),
```

```
    .LB_red(LB_red),
```

```
    .clk(clk)
```

```
);
```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
    SA = 0;
```

```
    SB = 0;
```

```
    #10;
```

```
    assert(LA_green && LB_red);
```

```
    SA = 1;
```

```
    #10;
```

```
    assert(LA_yellow && LB_red);
```



```

    SA = 0;
    SB = 1;
    #10;
    assert(LB_green && LA_red);

    SA = 1;
    #10;
    assert(LA_red && LB_red);

    $finish;
end

endmodule

```

Counter

```

module BCD_Counter(
    input clk,
    input reset,
    input enable,
    input load,
    input [3:0] D,
    output [3:0] Q
);

always @(posedge clk) begin
    if (reset) begin
        Q <= 4'b0000;
    end
end

```

```
end
  if (enable) begin
    if (load) begin
      Q <= D;
    end else begin
      if (Q == 4'b1001) begin
        Q <= 4'b0000;
      end else begin
        Q <= Q + 1;
      end
    end
  end
end
end
```

endmodule

testbench

```
module BCD_Counter_TB;
```

```
    input clk;
```

```
    input reset;
```

```
    input enable;
```

```
    input load;
```

```
    input [3:0] D;
```

```
    output [3:0] Q;
```

```
    BCD_Counter counter(
```

```
        .clk(clk),
```

```
        .reset(reset),
```

```
        .enable(enable),
```

```
.load(load),  
.D(D),  
.Q(Q)  
);
```

```
always #((CLK_PERIOD)/2) clk = ~clk;
```

```
initial begin
```

```
    clk = 0;
```

```
    reset = 0;
```

```
    enable = 0;
```

```
    load = 0;
```

```
    D = 0;
```

```
    #20 reset = 1;
```

```
    #20 reset = 0;
```

```
    #10 enable = 1;
```

```
    #20;
```

```
    assert(Q == 4'b0001) else ;
```

```
    #30;
```

```
    assert(Q == 4'b0000) ;
```

```
    D = 4'b1100;
```

```
    load = 1;
```

```
    #20;
```

```
    load = 0;
```

```
    assert(Q == 4'b1100) ;
```

```
    #20;  
    assert(Q == 4'b1101) ;  
$finish;  
end
```

```
endmodule
```

BCD Counter

```
module BCD_Counter(  
    input clk,  
    input reset,  
    input enable,  
    output [3:0] BCD  
);
```

```
always @(posedge clk) begin  
    if (reset) begin  
        BCD <= 4'b0000;  
    end else if (enable) begin  
        if (BCD == 4'b1001) begin  
            BCD <= 4'b0000;  
        end else begin  
            BCD <= BCD+1;  
        end  
    end  
end  
end
```

```
endmodule
```

```
module BCD_Counter_Reset_TB;
```

```
    input clk;
```

```
    inpt reset;
```

```
    input enable;
```

```
    output [3:0] BCD;
```

```
    BCD_Counter counter(
```

```
        .clk(clk),
```

```
        .reset(reset),
```

```
        .enable(enable),
```

```
        .BCD(BCD)
```

```
    );
```

```
    always #((CLK_PERIOD)/2) clk = ~clk;
```

```
    initial begin
```

```
        clk = 0;
```

```
        reset = 0;
```

```
        enable = 0;
```

```
        #20 reset = 1;
```

```
        #20 reset = 0;
```

```
        #10 enable = 1;
```

```
        #20;
```

```
        assert(BCD == 4'b0001) ;
```

```

    #30;
    assert(BCD == 4'b0000) ;

    #30;
    assert(BCD == 4'b0001) ;

    #200;
    assert(BCD == 4'b1001) ;

    #30;
    assert(BCD == 4'b0000) ;

    #30;
    assert(BCD == 4'b0001);
    $finish;
end

endmodule

```

Two digit

```

module TwoDigit_BCD_Counter(
    input clk,
    input reset,
    output [3:0] ones,

```

```
output [3:0] tens
```

```
);
```

```
always @(posedge clk) begin
```

```
    if(ones ==9) begin
```

```
ones <=0;
```

```
if(tens ==9) begin
```

```
tens <=0;
```

```
end
```

```
else begin
```

```
        tens <= tens+1;
```

```
    end
```

```
end
```

```
else begin
```

```
ones <=ones+1;
```

```
end
```

```
endmodule
```

Testbench

```
module TwoDigit_BCD_Counter_TB;
```

```
    reg clk;
```

```
    reg reset;
```

```
    wire [3:0] ones;
```

```
    wire [3:0] tens;
```

```
    TwoDigit_BCD_Counter counter(
```

```
.clk(clk),  
.reset(reset),  
.ones(ones),  
.tens(tens),  
);
```

```
always #((CLK_PERIOD)/2) clk = ~clk;
```

```
initial begin
```

```
    clk = 0;
```

```
    reset = 0;
```

```
    #20 reset = 1;
```

```
    #20 reset = 0;
```

```
    #10;
```

```
    assert(ones == 4'b0000 && tens 4'b0000);
```

```
    $finish;
```

```
end
```

```
endmodule
```