
 


Altay İlker Yiğitel
22203024
Section:01

Multiplexer Graphical Symbol:

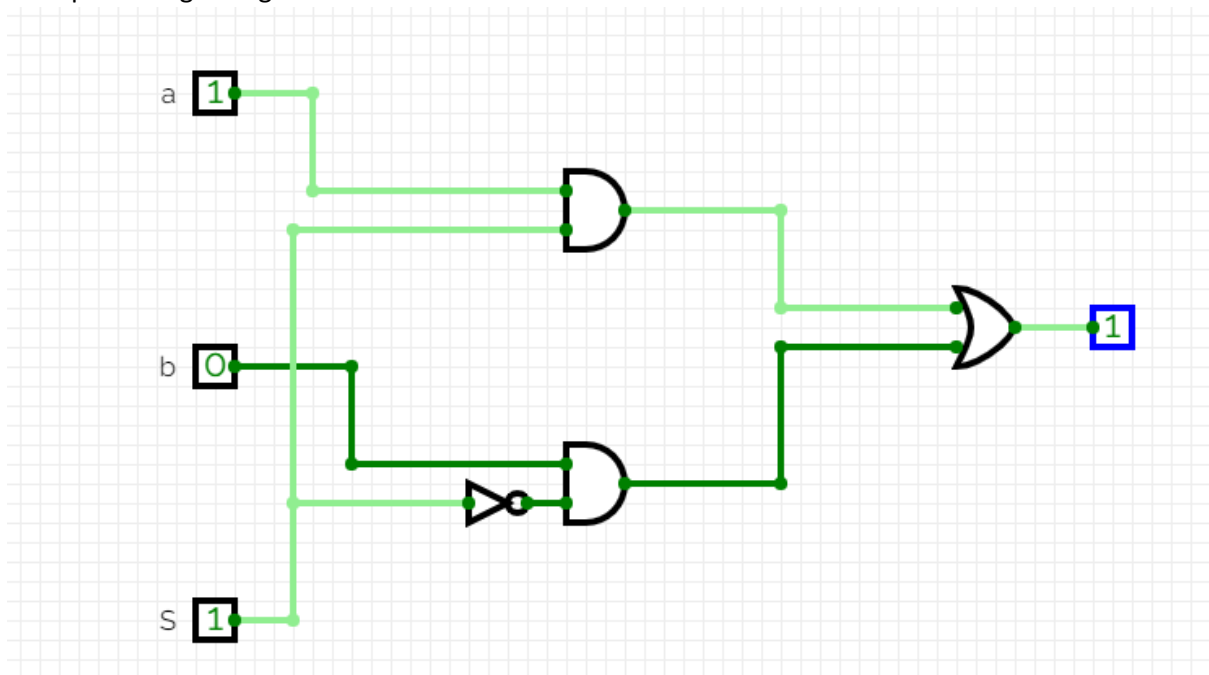

Multiplexer Logic Diagram :



Logic Diagram:

s	a	b	y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2-1 multiplexer behavioral module:

```

module mux-2-1(a,b,S0,y);
output y;
input a,b,S0;

assign y= (~S0 & a)|(S0&b);
endmodule

```

Testbench for 2-1 multiplexer:

```

module mux2_1_tb;

reg a, b, S0;
wire y;

mux_2_1 uut(a, b, S0, y);

initial begin
a = 0; b = 0; S0 = 0;
#100;

a = 0; b = 0; S0 = 1;
#100;

a = 0; b = 1; S0 = 0;
#100;

```

```

a = 0; b = 1; S0 = 1;
#100;

a = 1; b = 0; S0 = 0;
#100;

a = 1; b = 0; S0 = 1;
#100;


a = 1; b = 1; S0 = 0;
#100;

a = 1; b = 1; S0 = 1;
#100;

$finish();
end
endmodule

```

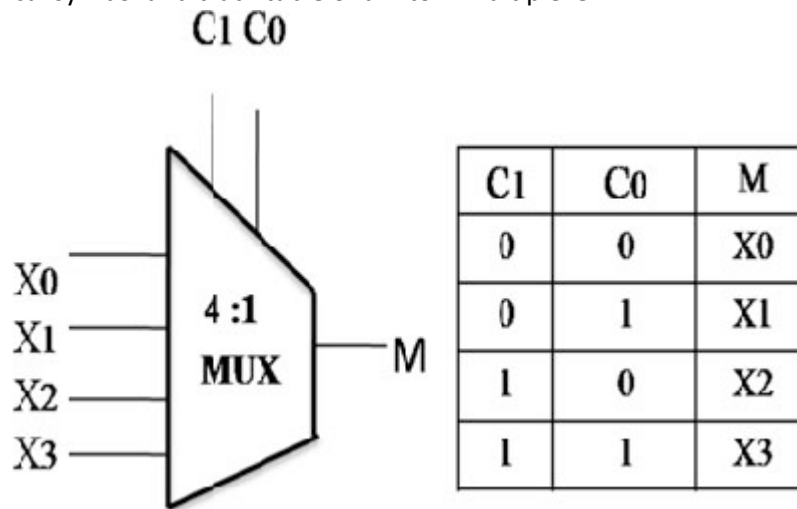Graphical symbol and truth table of a 4-to-1 multiplexer:



Behavioral SystemVerilog module for 4-to-1 multiplexer by using three 2-to-1 multiplexers:

```

module mux4_1(
    input a, b, c, d, S0, S1,
    output y2,
    wire y0, y1
);

assign y0 = (~S0 & a) | (S0 & b);
assign y1 = (~S1 & c) | (S1 & d);
assign y2 = ((S0 ^ S1) & y0) | ((~(S0 ^ S1)) & y1);

endmodule

```

Testbench:


```
module mux_4_1_tb();

reg a, b, c, d, S0, S1;
wire y0, y1, y2;
mux_4_1 uut (
.a(a),
.b(b),
.c(c),
.d(d),
.S0(S0),
.S1(S1),
.y0(y0),
.y1(y1),
.y2(y2);

initial begin
for (int i = 0; i < 64; i = i + 1) begin
a = i[5];
b = i[4];
c = i[3];
d = i[2];
S1 = i[1];
S0 = i[0];
#100;
end
$finish;
Endmodule
```


Three-input logic function g part a with single 4-to-1 multiplexer:

 When w1 is true and others are false 0 condition gives true output, 1 and 2 condition gives true only when w1 is false and one of w2 and w3 are true when all are true 3 condition is true so output is true as well.




Three-input logic function g part b with single 4-to-1 multiplexer:

 The function gives true when 2 or 3 of the switches are on so when controller is 0 both of the switches have to be 1 and when controller is 1 it doesn't matter whether one or two of them are true. 1 and 2 numbered inputs of multiplexer and second controller are unnecessary.



Three-input logic function g part b with single 2-to-1 multiplexer:

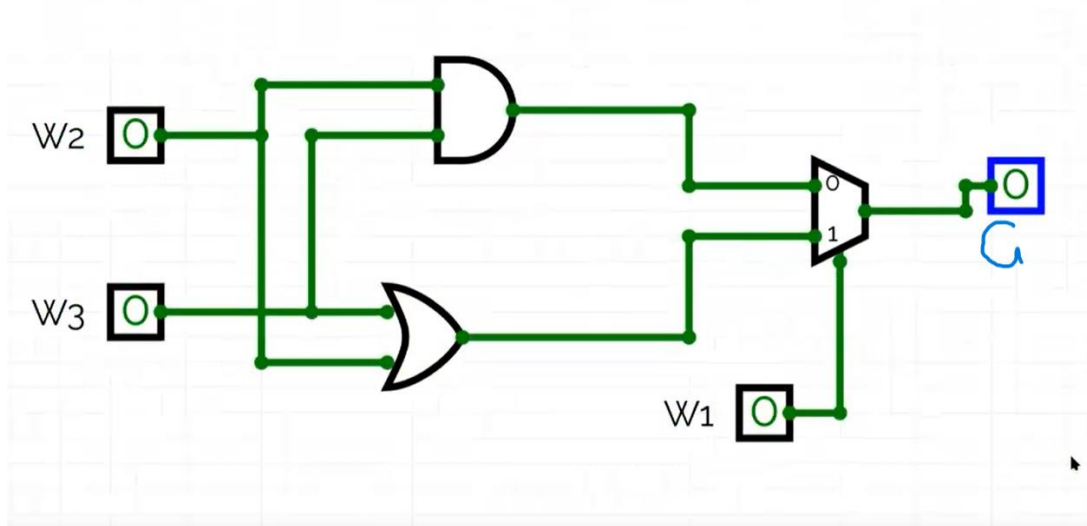And gate in the diagram limits w1 when it is 0 and only when w2 and w3 are both true it is true and for the or gate whenever w2 or w3 becomes true and w1 is true it gives true as an answer.



Behavioral SystemVerilog module for the function implemented with a 2-to-1 multiplexer:

```
module oneB(
  output y,
  input w1, w2, w3
);
```


```
assign y = (~w1 & (w2&w3)) | (w1 & (w2^w3));
```

```
endmodule
```


Testbench:

```
module oneB_tb;  
reg w1, w2, w3;  
wire y;  
oneB uut ( .w1(w1),  
.w2(w2),  
.w3(w3),  
.y(y) );  
w1 = 0; w2 = 0; w3 = 0;  
#10;  
w1 = 0; w2 = 0; w3 = 1;  
#10;  
w1 = 0; w2 = 1; w3 = 0;  
#10;  
w1 = 0; w2 = 1; w3 = 1;  
#10;  
w1 = 1; w2 = 0; w3 = 0;  
#10;  
w1 = 1; w2 = 0; w3 = 1;  
#10;  
w1 = 1; w2 = 1; w3 = 0;  
#10;  
w1 = 1; w2 = 1; w3 = 1;  
#10;  
$finish;  
end  
endmodule
```

Graphical symbol of a 2-to-4 decoder:

 

Logic diagram of a 2-to-4 decoder:

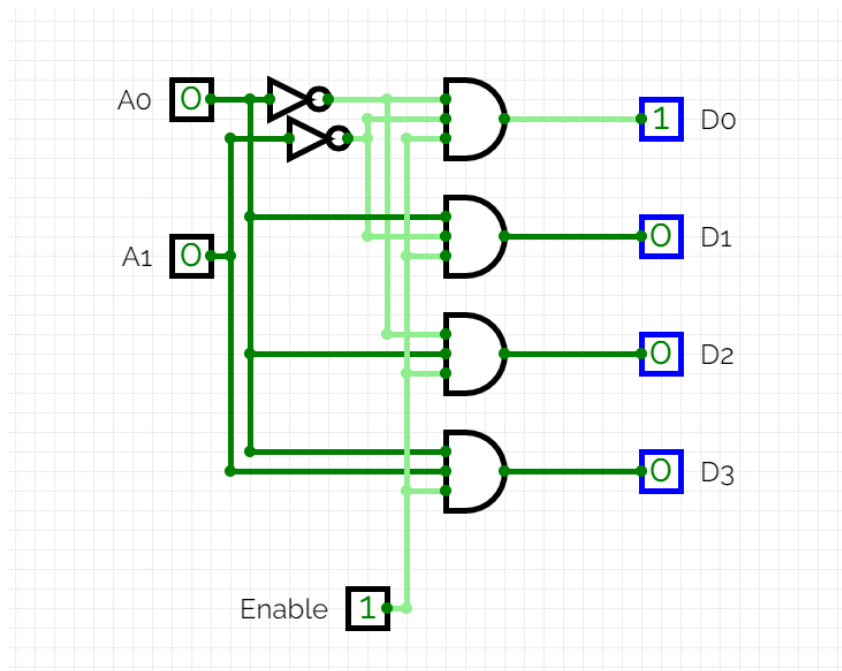

Truth table of a 2-to-4 decoder:

Inputs			Outputs			
EN	A	B	Y ₃	Y ₂	Y ₁	Y ₀
0	×	×	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Behavioral SystemVerilog module for 2-to-4 decoder:

```

module decoder4_2(a,b,en,y0,y1,y2,y3);
output y0,y1,y2,y3;
input a, b, en;

```

```

assign y0 = (en&(~a&~b));
assign y1 = (en&(a&~b));
assign y2 = (en&(~a&b));
assign y3 = (en&(a&b));

```

```
endmodule
```

Testbench:

```
module decoder4_2_tb;

reg a, b, en;

wire y0, y1, y2, y3;

decoder4_2 uut ( .a(a),
                .b(b),
                .en(en),
                .y0(y0),
                .y1(y1),
                .y2(y2),
                .y3(y3) );

initial begin
    a = 0; b = 0; en = 0;
    #100;

    a = 0; b = 0; en = 1;
    #100;

    a = 0; b = 1; en = 0;
    #100;

    a = 0; b = 1; en = 1;
    #100;

    a = 1; b = 0; en = 0;
    #100;

    a = 1; b = 0; en = 1;
    #100;

    a = 1; b = 1; en = 0;
    #100;

    a = 1; b = 1; en = 1;
    #100;

    $finish();
end
```




```

end
endmodule

```

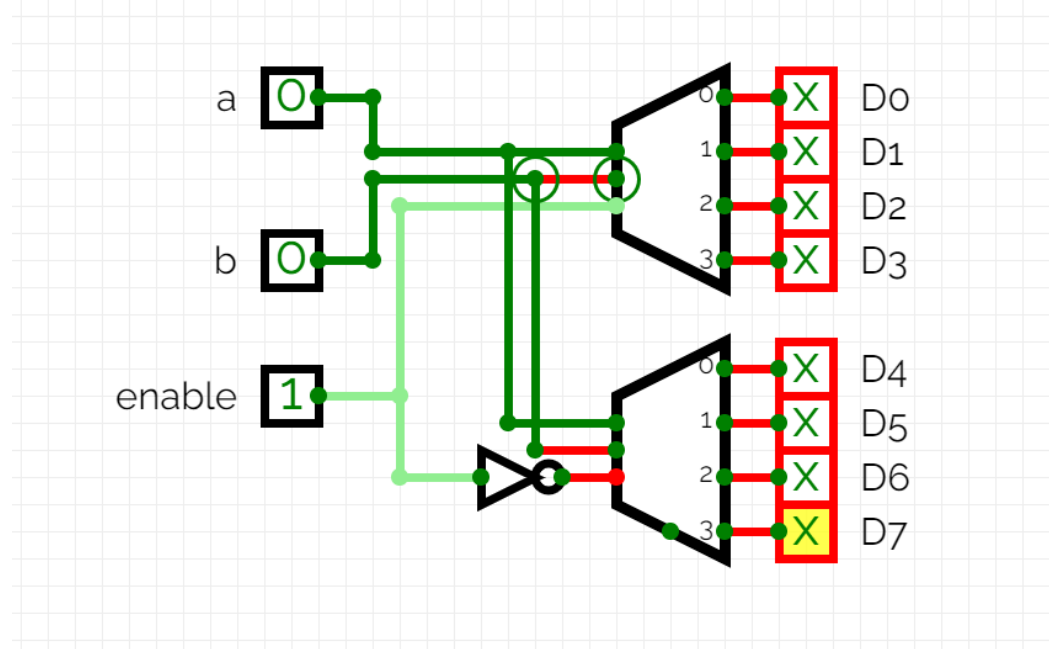Logic diagram of 3-to-8 decoder using 2-to-4 decoders and minimal amount of gates:



Structural SystemVerilog module for 3-to-8 decoder using 2-to-4 decoders:

```

module decoder8_3();
output y0,y1,y2,y3,y4,y5,y6,y7;
input a,b,en;

```

```

assign y0 = (en&(~a&~b));
assign y1 = (en&(a&~b));
assign y2 = (en&(~a&b));
assign y3 = (en&(a&b));

```

```

assign y4 = (~en&(~a&~b));
assign y5 = (~en&(a&~b));
assign y6 = (~en&(~a&b));
assign y7 = (~en&(a&b));

```

```

endmodule

```

Testbench:

```
module decoder8_3_tb;
reg a, b, en;
wire y0, y1, y2, y3,y4,y5,y6,y7;
decoder8_3 uut ( .a(a),
.b(b),
.en(en),
.y0(y0),
.y1(y1),
.y2(y2),
.y3(y3)
.y4(y4),
.y5(y5),
.y6(y6),
.y7(y7),);
initial begin
    a = 0; b = 0; en = 0;
    #100;

    a = 0; b = 0; en = 1;
    #100;

    a = 0; b = 1; en = 0;
    #100;

    a = 0; b = 1; en = 1;
    #100;

    a = 1; b = 0; en = 0;
    #100;

    a = 1; b = 0; en = 1;
    #100;

    a = 1; b = 1; en = 0;
    #100;
```


```

a = 1; b = 1; en = 1;
#100;

$finish();
end
Endmodule

```

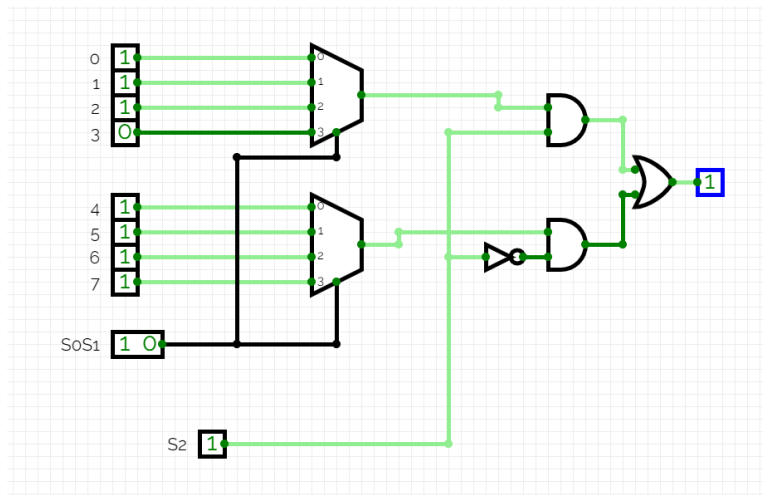Schematic (block diagram) of 8-to-1 MUX by using two 4-to-1 MUX modules:



SystemVerilog module of 8-to-1 MUX :

```

module mux8_1(

    input a, b, c, d,e,f,g,h ,S0, S1,S2,

    output y6

);

//mux4_1
assign y0 = (~S0 & a) | (S0 & b);

assign y1 = (~S1 & c) | (S1 & d);

assign y2 = ((S0 ^ S1) & y0) | ((~(S0 ^ S1)) & y1);
//mux4_1_2
assign y3 = (~S0 & e) | (S0 & f);

assign y4 = (~S1 & g) | (S1 & h);

assign y5 = ((S0 ^ S1) & y3) | ((~(S0 ^ S1)) & y4);

```

```
assign y6 = (y2&S2)^(y5&~S2);
```

```
endmodule
```

Testbench:

```
module mux8_1_tb;
```

```
reg a, b, c, d, e, f, g, h;
```

```
reg S0, S1, S2;
```

```
wire y6;
```

```
module mux8_1 dut ( .a(a), .b(b), .c(c), .d(d), .e(e), .f(f), .g(g), .h(h), .S0(S0), .S1(S1), .S2(S2), .y6(y6) );
```

```
initial begin
```

```
S0=0, S1=0, S2=0 {a, b, c, d, e, f, g, h} = 8'b00000000;
```

```
{S0, S1, S2} = 3'b000;
```

```
#10;
```

```
S0=0, S1=0, S2=1 {S0, S1, S2} = 3'b001;
```

```
#10;
```

```
S0=0, S1=1, S2=0 {S0, S1, S2} = 3'b010;
```

```
#10;
```

```
S0=0, S1=1, S2=1 {S0, S1, S2} = 3'b011;
```

```
#10;
```

```
S0=1, S1=0, S2=0 {S0, S1, S2} = 3'b100;
```

```
#10;
```

```
S0=1, S1=0, S2=1 {S0, S1, S2} = 3'b101;
```

```
#10;
```

```
S0=1, S1=1, S2=0 {S0, S1, S2} = 3'b110;
```

```
#10;
```

```
S0=1, S1=1, S2=1 {S0, S1, S2} = 3'b111;
```

```
#10;
```

```
$finish;
```

```
end
```

```
endmodule
```